

Critical Distance Detection using Ultrasonic Sensor:

Names:	ID	Team task
Ahmed Mostafa AbdEl-Rahman	20221372883	Forming circuit
Mazen Gaber Mahmoud	20221372110	Coding
AbdEL-Rahman Tarek Zaki	20221442265	Forming circuit
Louay Medhat Mohamed	20201447561	Coding

Steps of formation:

1. First : we connect the +5V and GND of Arduino UNO to the breadboard.
2. For LED: Connect cathode to the ground and Anode with a 220 ohm resistor. Connect the second pin of resistor with pin 6 of the Arduino.
3. For Buzzer: Connect the Positive terminal with pin 8 of Arduino and negative terminal to GND.
4. For Ultrasonic Sensor: Connect the VCC and GND, Connect the Trigger pin to pin 12 and Echo pin to pin 13 of Arduino.

Now we have finished forming circuit.

Note: The maximum distance measured by it 30cm.

