

Names:

- **Abdelrhman Mohamed Abdelhady Hodib 2022513643**
- **Antonios Gerges Nageh 20221903971**
- **Abdelrhman Ahmed Fathy 20221441784**
- **Hashem Ahmed Abdelhafiz 20221445676**
- **Hussien Hesham Ibrahim 20221372791**
- **Youssef Ibrahim Shehata 2103127**


Steps of formation:

1. First: we connect the +5V and GND of Arduino UNO to the breadboard.
2. For LED: Connect cathode to the ground and Anode with a 330 ohm resistor. Connect the second pin of resistor with pin 6 of the Arduino.
3. For Buzzer: Connect the Positive terminal with pin 8 of Arduino and negative terminal to GND.
4. For Ultrasonic Sensor: Connect the VCC and GND, Connect the Trigger pin to pin 12 and Echo pin to pin 13 of Arduino.


Now we have finished forming circuit.

Note: The Specified distance to detect is 20 cm.

Photo of TinkerCad:

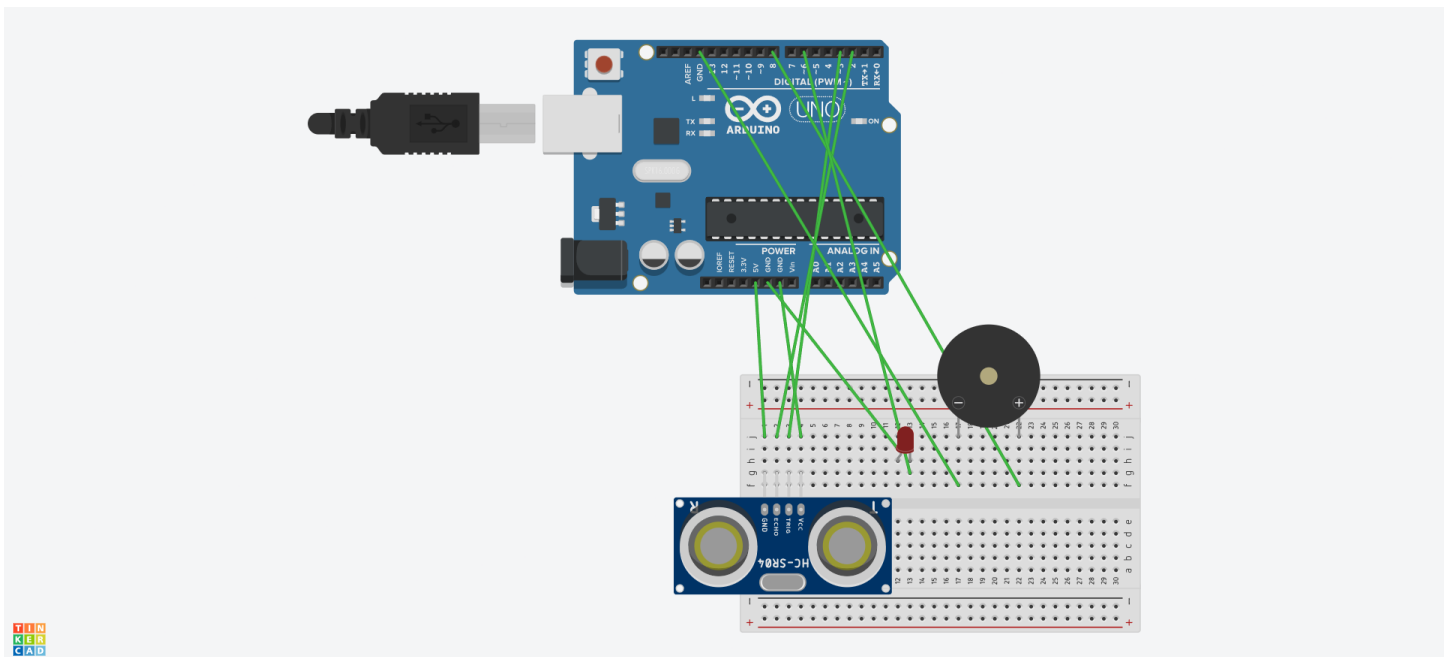

Schematic View:

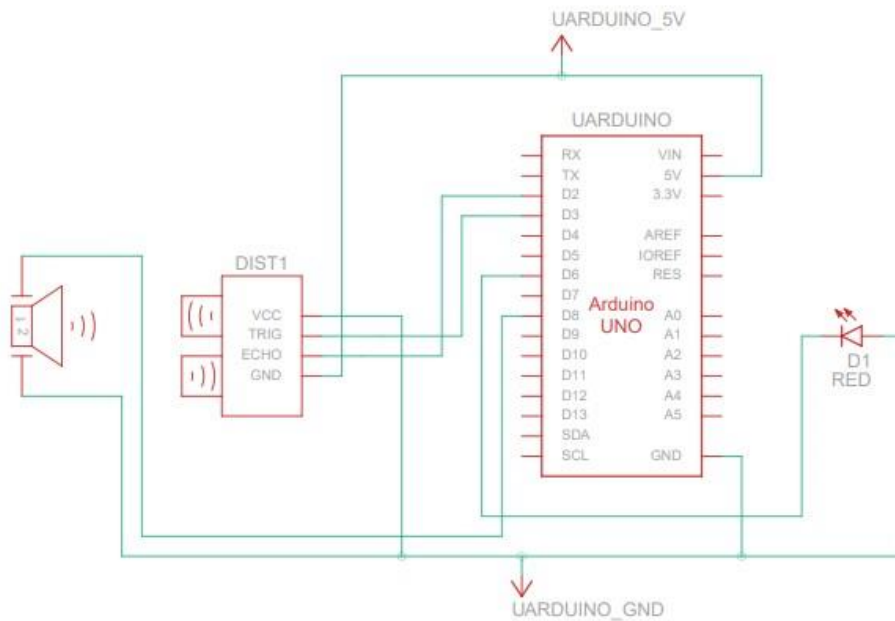

Tasks:

Name	Task
Abdelrhman Mohamed	Forming circuit
Abdelrhman Fathy	Forming circuit
Antonios Gerges	Coding
Youssef Ibrahim	Coding
Hussein Hashem	Writing Report
Hashem Ahmed	Tinkercad